

Two-by-Two Linear Systems through Kirchhoff Circuits

Turn two familiar circuit equations into a small linear system that can be solved, checked, and interpreted.


Physical question. Two resistor loops share one resistor. If the source voltages and resistances are known, how can we find the two loop currents without losing track of signs, units, or physical meaning?

Core learning outcomes

1. derive two consistent Kirchhoff equations from a stated current convention;
2. map those equations to $A\mathbf{x} = \mathbf{b}$ and solve them with MATLAB backslash; and
3. validate the solution by direct substitution and interpret the current signs physically.

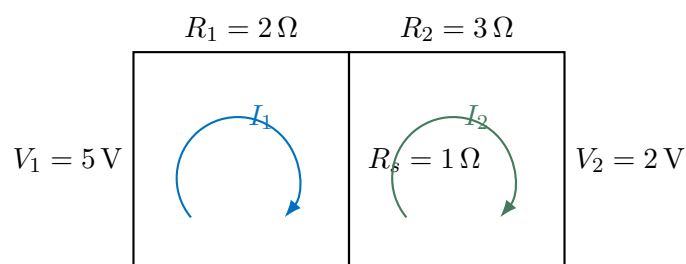1. Start from the circuit, not the matrix

Choose both mesh currents clockwise. Let the left private resistor be $R_1 = 2\ \Omega$, the right private resistor $R_2 = 3\ \Omega$, and the shared resistor $R_s = 1\ \Omega$. The source rises are $V_1 = 5\ \text{V}$ and $V_2 = 2\ \text{V}$.



Across the shared resistor, the two mesh currents oppose each other. If we define the shared-branch direction to follow mesh 1, then

$$I_{\text{shared}} = I_1 - I_2.$$

Prediction checkpoint. Both chosen mesh-current directions should give positive currents. The larger source and smaller private resistance suggest $I_1 > I_2$.

2. Write Kirchhoff equations in words first

For the left loop: *left private voltage drop plus shared-resistor voltage drop equals the left source rise.* Therefore

$$R_1 I_1 + R_s (I_1 - I_2) = V_1,$$

or

$$(R_1 + R_s) I_1 - R_s I_2 = V_1.$$

For the right loop, the shared-resistor contribution is reversed:

$$-R_s I_1 + (R_2 + R_s) I_2 = V_2.$$

Every term has units of volts because $\Omega \times \text{A} = \text{V}$.

3. Map each equation to one matrix row

The two equations become

$$\begin{bmatrix} R_1 + R_s & -R_s \\ -R_s & R_2 + R_s \end{bmatrix} \begin{bmatrix} I_1 \\ I_2 \end{bmatrix} = \begin{bmatrix} V_1 \\ V_2 \end{bmatrix}.$$

With the locked values,

$$\underbrace{\begin{bmatrix} 3 & -1 \\ -1 & 4 \end{bmatrix}}_{A \text{ } (\Omega)} \underbrace{\begin{bmatrix} I_1 \\ I_2 \end{bmatrix}}_{\mathbf{x} \text{ (A)}} = \underbrace{\begin{bmatrix} 5 \\ 2 \end{bmatrix}}_{\mathbf{b} \text{ (V)}}.$$

Key idea. A matrix is only a compact storage format for the two physical equations. Every coefficient must be traceable back to one Kirchhoff term.

4. Pseudocode before MATLAB

1. store the resistances and source voltages;
2. build one matrix row from each Kirchhoff equation;
3. store the two source voltages in a column vector;
4. solve the two unknown currents;
5. reconstruct the shared-branch current;
6. substitute the currents back into both original equations; and
7. interpret the current signs and magnitudes.

5. Solve the supplied system in MATLAB

```
1 R1_ohm = 2; R2_ohm = 3; Rs_ohm = 1;  
2 V1_V = 5; V2_V = 2;  
3 A_ohm = [R1_ohm+Rs_ohm, -Rs_ohm; ...  
4         -Rs_ohm, R2_ohm+Rs_ohm];  
5 b_V = [V1_V; V2_V];  
6 x_A = A_ohm\b_V;  
7 I1_A = x_A(1);  
8 I2_A = x_A(2);
```

The solution is $I_1 = 2 \text{ A}$ and $I_2 = 1 \text{ A}$. The reconstructed shared-branch current is

$$I_{\text{shared}} = 2 - 1 = 1 \text{ A}.$$

6. Core validation: substitute into the original equations

For the left equation,

$$3(2) - 1(1) = 5 \text{ V},$$

which reproduces the 5 V source. For the right equation,

$$-1(2) + 4(1) = 2 \text{ V},$$

which reproduces the 2 V source.

```
1 left_V = (R1_ohm+Rs_ohm)*I1_A - Rs_ohm*I2_A;  
2 right_V = -Rs_ohm*I1_A + (R2_ohm+Rs_ohm)*I2_A;  
3 check_V = [left_V-V1_V; right_V-V2_V];  
4 assert(max(abs(check_V)) < 1e-12)
```

Validation result. Both reconstructed loop voltages match the original sources. This directly checks the equations that represent the circuit.

7. Interpret signs rather than fearing them

Both currents are positive, so the actual mesh currents follow the assumed clockwise arrows. If MATLAB had returned a negative value, that would not automatically mean the calculation failed; it would mean the actual current runs opposite to the arrow chosen before solving.

8. Diagnose a plausible wrong matrix

Suppose the first off-diagonal coefficient is accidentally entered as $+R_s$ instead of $-R_s$. MATLAB can still return numbers, but those currents no longer satisfy the correct physical equations. The right response is not “MATLAB worked”; it is to substitute the solution into the original Kirchhoff equations and inspect the mismatch.

Responsible-AI caution. An AI-generated matrix can be syntactically perfect and physically wrong. Before accepting it, trace each coefficient to the stated current direction and Kirchhoff equation, then validate the solved currents independently.

Working exposure: equivalent equation ordering

Swapping the two equation rows is harmless only if the same swap is applied to both A and $\mathbf{b}$. The physical system is unchanged because the two equations are merely listed in a different order.

Working exposure: sensitivity intuition

If the right source changes slightly from 2.0 V to 2.1 V, both currents change because the loops are coupled through the shared resistor. At this stage, notice the coupling qualitatively; formal conditioning belongs to stretch work.

Optional stretch: residual, rank, conditioning, and power

Advanced diagnostics include the residual $A\mathbf{x} - \mathbf{b}$, ‘rank(A)’, and ‘cond(A)’. A second physical check for this resistor circuit is source power versus resistor dissipation. These are useful distinction-level extensions, but they are not required for the Core Week 3 route.

Three takeaways

1. Choose unknown directions and derive the Kirchhoff equations before constructing a matrix.
2. Each row of $A\mathbf{x} = \mathbf{b}$ must preserve both the physical sign convention and the units.
3. A solver result becomes credible only after direct substitution and physical interpretation.

Preparation for the practical. Be ready to transfer the same workflow to another two-loop circuit and to a two-node KCL model. For each case, state the unknowns and units, map the equations to $A\mathbf{x} = \mathbf{b}$, solve with backslash, and validate the original equations before trusting the result.